



# Chapter 4

## Voltage, Current, and Power

Voltage and Current  
Resistance and Ohm's Law  
AC Voltage and Power



**ARRL** *The national association for  
AMATEUR RADIO*


# E, I, and R in a Series Circuit

A circuit is a closed path.

E represents the voltage in the circuit – a battery.

I represents the current in the circuit – the same at all points.

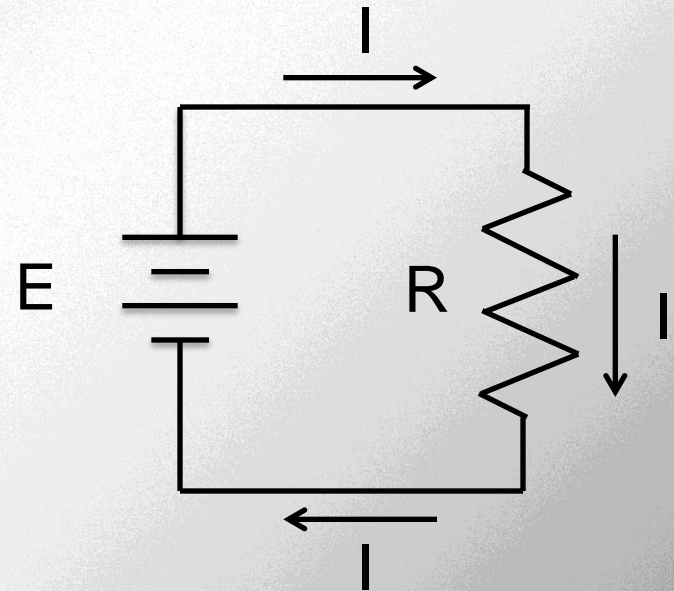
R represents the resistance of the circuit.


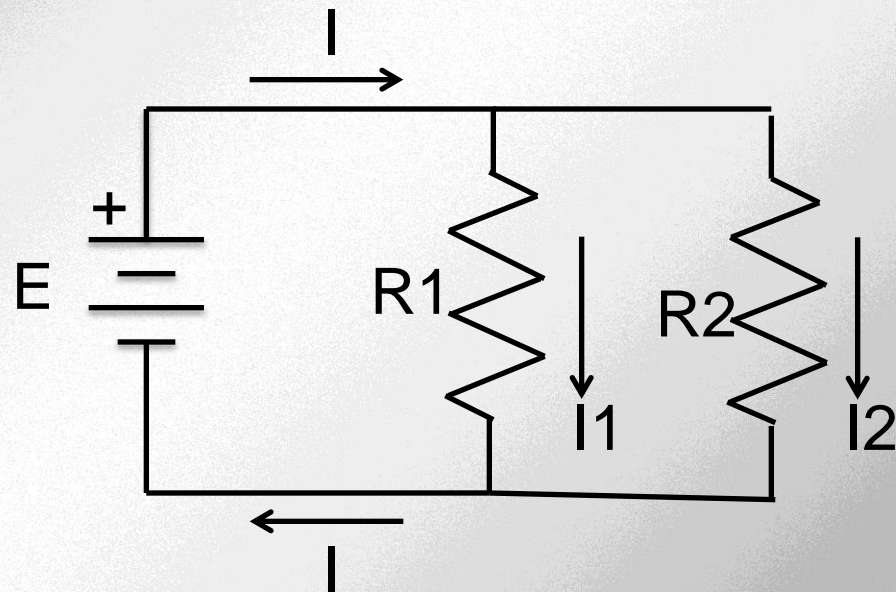
# Currents in a Parallel Circuit

When two or more resistors are in parallel, each resistor takes part of the current  $I$ .

$I = I_1 + I_2$  is part of Kirchoff's Law.



$$I = I_1 + I_2$$





# Ohm's Law ( $E = I * R$ )

Ohm's Law is the proportional relationship between Voltage and Current.

Current is proportional to diameter of conductor but inversely proportional to length of conductor.

- Larger conductor – More current for a given voltage.
- Longer conductor – More voltage for same current.



**ARRL** *The national association for  
AMATEUR RADIO*



# Ohm's Law

A picture to remember  
Ohm's Law


- E is voltage – Volts
- I is current – Amperes
- R is resistance – Ohms

Cover the one you don't  
know:

$$E = I R$$

$$I = E \text{ Over } R$$

$$R = E \text{ Over } I$$

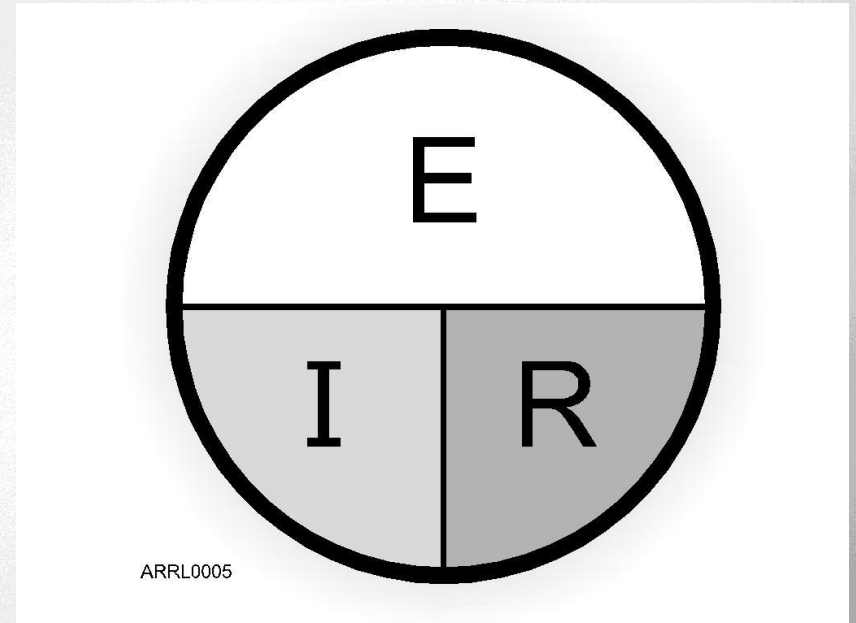

One Ohm, one Amp, one Volt



# Basic Types of Current

## Direct Current (DC)

- Electrons move in one direction.
- Can fluctuate (pulse or ripple) in magnitude, but still only in one direction.

## Alternating Current (AC)

- Electrons reverse direction at a frequency.
- Current goes from zero to positive to zero to negative to zero .....

AC and DC may be mixed together.

AC may be sinewave, pulse, triangle, random ...



# Alternating Current Defined

An Alternating Voltage reverses polarity periodically in a cycle from positive to negative.

- The alternating voltage forces charges (electrons) to move back and forth through the conductor.
- The current is called Alternating Current or AC.
- The combination of a Positive period and a Negative period is called a Cycle.
- Frequency is the number of cycles in one second. (Hertz or Hz)




**ARRL** The national association for  
AMATEUR RADIO





# AC Vocabulary

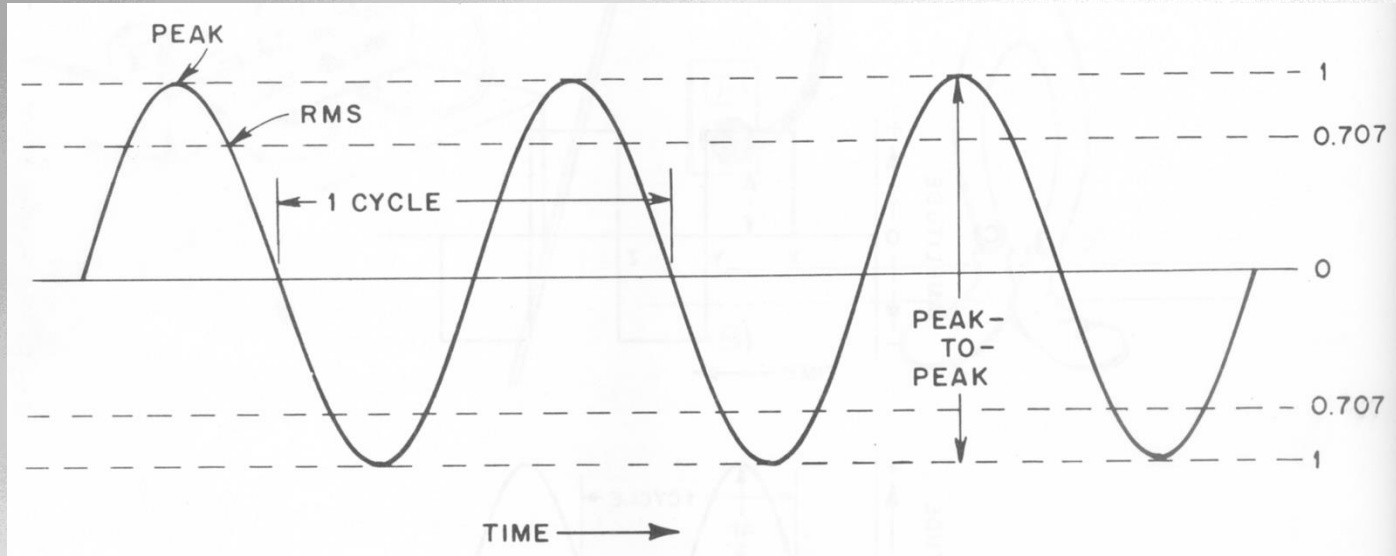

This AC Voltage is a Sine Wave.  
Other AC Voltages may be rectangular or  
triangular or irregular shapes.



**ARRL** The national association for  
AMATEUR RADIO





# Electrical Power

Power (Watts) is the rate of doing work. Work is equivalent to Energy (Joules). Work is basically the effort expended to move a mass.

- Movement caused by a Force over a distance.
- Movement caused by a Pressure over a distance.


If something doesn't move, there is no work produced.

Heat produced is also a measure of work.

Power can be different at different points of a circuit.



# Memory Device for Power Formula

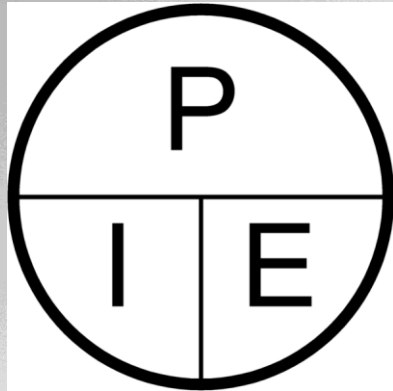


The Pie Chart – Cover the one you want.

- Cover P:  $P = I * E$
- Cover I:  $I = P / E$
- Cover E:  $E = P / I$

One Volt, One Amp, One Watt



# Other Formulas for Power

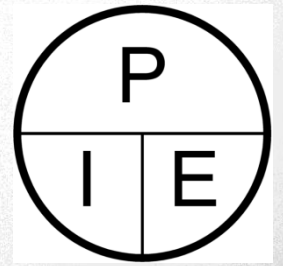

$P = I * E$  works when you know  $I$  and  $E$ . But if you only know  $E$  and  $R$  or  $I$  and  $R$  you can do some substitution.


1)  $P = I * E$ ; 2)  $E = I * R$ ; 3)  $I = E/R$

- Substitute  $I * R$  for  $E \rightarrow P = I * (I * R) \rightarrow P = I^2 R$
- Substitute  $E/R$  for  $I \rightarrow P = E * (E/R) \rightarrow P = E^2/R$
- Use  $P = I^2 R$  when you know  $I$  and  $R$ .
- Use  $P = E^2/R$  when you know  $E$  and  $R$ .





# DC Power vs. AC Power

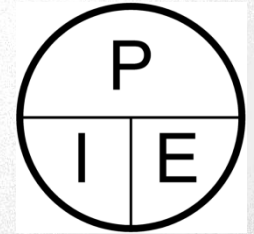

$P = I * E$  works for DC circuits where voltage and current are constant.

- 12 Volts pushing 2 Amps = 24 Watts
- 1.5 Volts pushing 300 mA = 450 mW

But in an AC circuit, the voltage and current are constantly changing.

- Power at an instant is voltage at that instant times current at that instant.
- Sometimes the power is zero and sometimes it is maximum.



# Effective Voltage for AC Power

The voltage used for power calculations in AC is the equivalent dc voltage value that would do the same amount of work (or heat).

- A simple average of AC voltage is lower than the effective value.
- The effective voltage is a weighted average called Root Mean Square (RMS).



# Important Points about RMS

- **For Sine Waves Only**, the RMS voltage is 0.707 times the peak voltage!!!!
- AC voltmeters may indicate RMS voltage, but value may be wrong if wave is distorted.
- Some Digital Multimeters measure *True RMS* and are more accurate on distorted waves.





# Converting Peak Voltage to RMS

$$V_{Peak} = 1.414(V_{RMS})$$

$$V_{RMS} = \frac{V_{Peak}}{1.414} = .707(V_{Peak})$$

$$V_{P-to-P} = 2(V_{Peak})$$

Remember:

1.414 = Square root of 2

0.707 = 1 / Square root of 2



**ARRL** The national association for  
AMATEUR RADIO



# Peak Envelope Power

Peak Envelope Power, PEP, is the power based on the highest Peak Voltage.

Sometimes we know the R and can measure  $V_{PK-PK}$  on an oscilloscope.

Convert Peak or Peak-to-Peak voltage to RMS.  
Then:

$$PEP = \frac{(V_{RMS})^2}{R}$$



# Using Decibels

Decibels (dB) are used to compare power levels and gains or losses in a system.

- Gains and losses of a system in dB are additive.
- Decibels are logarithmic.
- Matches the physical responses of hearing and sight.
- A large range of decades of values can be compared with smaller numbers, i.e., a Gain of 1,000,000 is 60dB, 1,000 is 30dB, 100 is 20dB

Commonly used to compare input to output power.

Positive → Gain; Negative → Loss.





# dB and Power Ratio Calculations

If you know the powers at two points, P2 and P1, in a system, you can calculate the gain in dB.

$$\text{Gain as a ratio: } \mathit{Gain} = \frac{P_2}{P_1}$$

$$\text{Gain in db: } G_{db} = 10 \log_{10}(\mathit{Gain})$$

$$G_{db} \text{ to ratio: } \mathit{Gain} = 10^{\frac{G_{db}}{10}} = \frac{P_2}{P_1}$$



# G5B05

How many watts are dissipated when a current of 10.4 milliamperes flows through 1.0 kilohms resistance?

- A. Approximately 108 milliwatts
- B. Approximately 10.8 Watts
- C. Approximately 10.4 Watts
- D. Approximately 10.4 milliwatts

Answer: A



# Solution

$$P = I^2 R ; (I \text{ Squared } R)$$

$$I = 10.4 * 10^3 \text{ Amps} ; (10.4 \text{ E-3})$$

$$R = 1.0 * 10^3 \text{ Ohms} ; (1.0 \text{ E3})$$

$$P = (10.4 \text{ E-3})^{**2} * 1.0 \text{ E3}$$

$$P = 1.08 \text{ E-4} * 1.0 \text{ E3}; (E-4 * E3 = E-1)$$

$$P = 1.08 \text{ E-1} = 108 \text{ E-3 Watts}$$

$$\underline{P \sim 108 \text{ mW}}$$



# G5B06

What is the output PEP from a transmitter if an oscilloscope measures 200 volts peak-to-peak across a 50 ohm dummy load connected to the transmitter output?

A. 1.4 watts

B. 100 watts

C. 353.5 watts

D. 400 watts

Answer: B



# Solution

$$V_{pk-pk} = 200V$$

$$R = 50\text{ohms}$$

$$V_{pk} = V_{pk-pk}/2 = 200V/2 = \underline{100V}$$

$$V_{rms} = 0.707 * V_{pk} = 0.707 * 100 = \underline{70.7V}$$

$$PEP = V_{rms}^2/R$$

$$PEP = (70.7V)^2 / 50\text{ohms} = 5000V^2 / 50\text{ohms}$$

$$PEP = \underline{100W}$$



# G5B07

What value of an AC signal produces the same power dissipation in a resistor as a DC voltage of the same value?

- A. The peak-to-peak value
- B. The peak value
- C. The RMS value
- D. The reciprocal of the RMS value

Answer: C



# G5B09

What is the RMS voltage of a sine wave with a value of 17 volts peak?

- A. 8.5 volts
- B. 12 volts
- C. 24 volts
- D. 34 volts

Answer: B



# G5B10

What percentage of power loss would result from a transmission line loss of 1 dB?

- A. 10.9 percent
- B. 12.2 percent
- C. 20.5 percent
- D. 25.9 percent

Answer: C



# Solution

$$\text{DB} = -1 = 10 \text{ Log}(G)$$

$$\text{Log}(G) = -1/10 = -0.1$$

$$G = \text{AntiLog} (-0.1) = 10^{-0.1} = 0.794$$

$$\text{Loss} = 1 - 0.794 = 0.205$$

$$\% \text{Loss} = 100 * \text{Loss} = 100 * 0.205 = 20.5\%$$

If you can remember that a gain of 1DB is 1.26 times, then the power after the loss is  $1/1.26 = 0.793$  so the loss is  $\sim 0.20$  or 20%.



**ARRL** The national association for  
AMATEUR RADIO





# G5B11

What is the ratio of peak envelope power to average power for an unmodulated carrier?

A.0.707

B.1.00


C.1.414

D.2.00


Answer: B




# Audio Signal

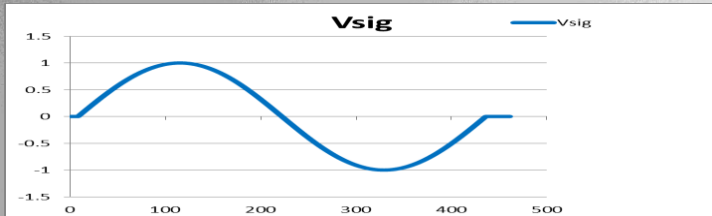


# Unmodulated RF

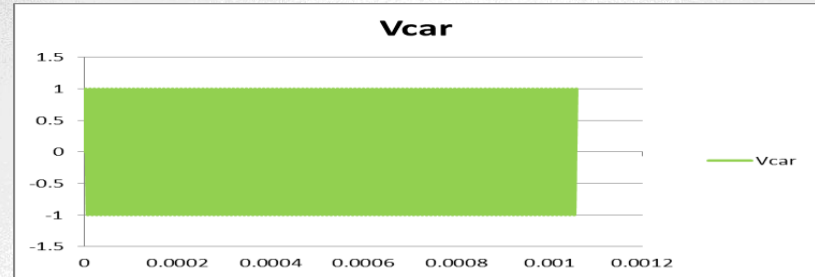

# AM with Carrier

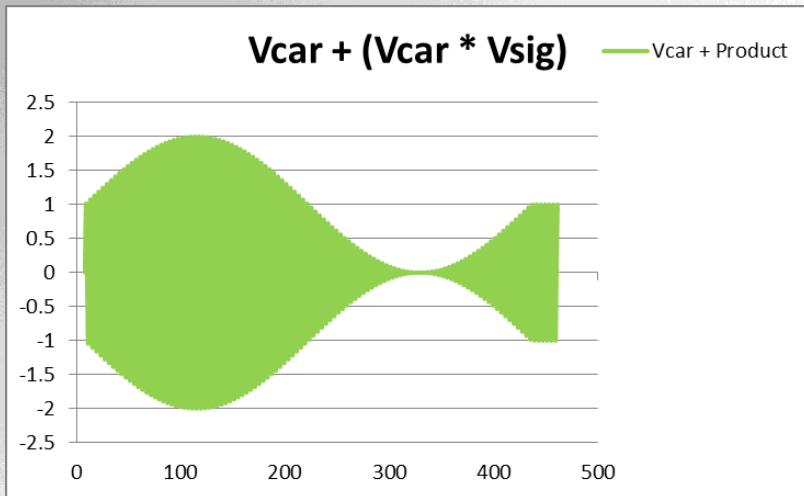

# AM With No Carrier

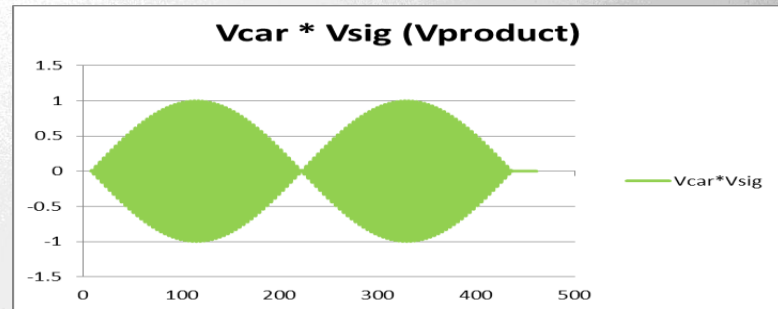

**ARRL** The national association for  
AMATEUR RADIO



# G5B12

What would be the RMS voltage across a 50 ohm dummy load dissipating 1200 watts?

- A. 173 volts
- B. 245 volts
- C. 346 volts
- D. 692 volts

Answer: B





# Solution

$$P = 1200W$$

$$R = 50 \text{ Ohms}$$

$$P = I * E; I = E/R; P = (E/R) * E$$

$$P = E * E/R = E^2/R$$

$$P * R = E^2$$

$$E = \text{Square Root } (P * R)$$

$$E = \text{Square Root}(1200 * 50)$$

$$E = 244.9 \text{ V}$$



# G5B13

What is the output PEP of an unmodulated carrier if an average reading wattmeter connected to the transmitter output indicates 1060 watts?

- A. 530 watts
- B. 1060 watts
- C. 1500 watts
- D. 2120 watts

Answer: B

# G5B14

What is the output PEP from a transmitter if an oscilloscope measures 500 volts peak-to-peak across a 50 ohm resistive load connected to the transmitter output?

- A. 8.75 watts
- B. 625 watts
- C. 2500 watts
- D. 5000 watts

Answer: B





# Solution

$$V_{pk-pk} = 500V$$

$$R = 50\text{ohms}$$

$$V_{pk} = V_{pk-pk}/2 = 500V/2 = \underline{250V}$$

$$V_{rms} = 0.707 * V_{pk} = 0.707 * 250 = \underline{176.75V}$$

$$PEP = V_{rms}^2/R$$

$$PEP = (176.75V)^2 / 50\text{ohms} = 31240.6V^2 / 50\text{ohms}$$

$$PEP = \underline{624.8W}$$